

07/07/2023

# 6872 Foundations of Electronics

## Lecture 11: Operational Amplifier (Op-Amp)

Elvio J. Leonardo

Bachelor Degree in Computer Science  
Department of Informatics  
State University of Maringá

v. 2020

# Abstract

- ▶ Op-Amp Basics
- ▶ Circuits
  - ▶ Inverting Amplifier
  - ▶ Summing Amplifier
  - ▶ Non-Inverting Amplifier
  - ▶ Unit Gain Amplifiers
  - ▶ Integrator
  - ▶ Differentiator
- ▶ Op-Amp Specifications
- ▶ Application Examples



Op Amp  $\rightarrow$  Idealizado para ter  
amplificações ideal:

- ganho infinito
- banda de amplificações infinita
- impedância de entrada infinita
  - $\hookrightarrow$  Não consome potência da fonte
  - $\hookrightarrow$  Funciona em baixíssimas correntes
- impedância de saída igual a zero

Sensores  $\left\{ \begin{array}{l} \text{médicos} \\ \text{agrícolas} \end{array} \right\}$  Op Amp é usado em áreas  
em que sinais muito baixos  
são gerados, para amplificá-los.
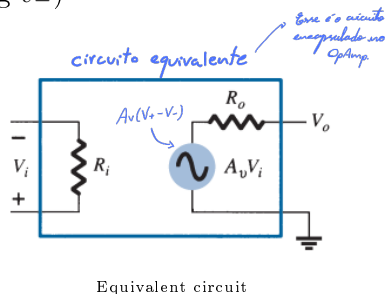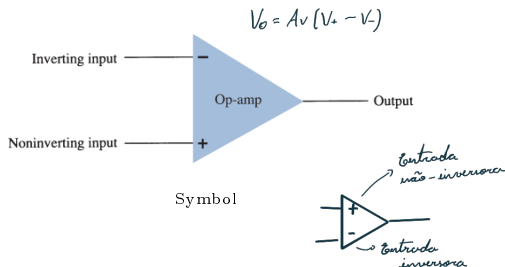
# Op-Amp Basics

- ▶ Op-Amp is an ideal amplifier having:
  - ▶ Infinite (open-loop) voltage gain  $A_v$  (actual: few thousands to tens of thousands)
  - ▶ Infinite bandwidth (actual: MHz to tens of MHz)
  - ▶ Infinite input impedance  $R_i$  (actual: few megohms)
  - ▶ Zero output impedance  $R_o$  (actual: less than  $100\ \Omega$ )
- ▶ Inputs (non-inverting  $v_+$  and inverting  $v_-$ )
- ▶ Output:  $V_o = A_v V_i = A_v(V_+ - V_-)$



# Inverting Amplifier

→ Amplificador Inversor

- Assuming  $R_i = \infty$  and  $R_o = 0$ :

$$i = \frac{V_i - V_-}{R_1} = -\frac{V_o - V_-}{R_f} \quad \underbrace{\frac{V_i - V_-}{R_1}}_{i_1} + \underbrace{\frac{V_o - V_-}{R_f}}_{i_f} = 0$$

$$V_o = A_v(V_+ - V_-) = -A_v V_- \rightarrow V_- = -\frac{V_o}{A_v}$$

- If  $A_v \gg 1$

$$V_- = -\frac{V_o}{A_v} \approx 0 \text{ (virtual ground)}$$


$$i = \frac{V_1}{R_1} = -\frac{V_o}{R_f}$$

$A_v \rightarrow$  ganho de tensão

Quando  $V_o$  tende ao infinito,  $A_v$  tende a zero.

- Output voltage:

$$V_o = -\frac{R_f}{R_1} V_1$$

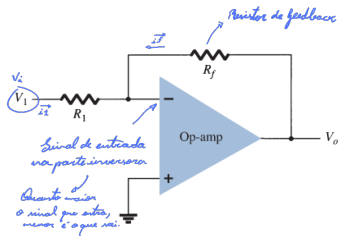

- Example:** If  $R_1 = 100 \text{ k}\Omega$  and  $R_f = 500 \text{ k}\Omega$  in the above figure, what output voltage results for an input of  $V_1 = 2 \text{ V}$ ?

$$V_o = -\frac{R_f}{R_1} V_1 = -\frac{500\text{k}}{100\text{k}} \times 2 = -10 \text{ V}$$

# Summing Amplifier

→ Amplificador somador

- Assuming  $R_i = \infty$  and  $R_o = 0$ :

$$i = \frac{V_1 - V_-}{R_1} + \dots + \frac{V_n - V_-}{R_n} = -\frac{V_o - V_-}{R_f}$$

$$V_o = A_v(V_+ - V_-) = -A_v V_- \rightarrow V_- = -\frac{V_o}{A_v}$$


- If  $A_v \gg 1$

$$V_- = -\frac{V_o}{A_v} \approx 0 \text{ (virtual ground)}$$

$$i = \frac{V_1}{R_1} + \dots + \frac{V_n}{R_n} = -\frac{V_o}{R_f}$$

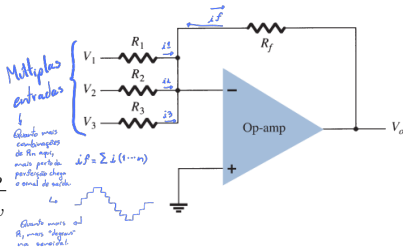- Example:** If  $R_f = 1 \text{ M}\Omega$  and  $V_1 = -2 \text{ V}$ ,  $V_2 = +3 \text{ V}$ ,  $V_3 = +1 \text{ V}$ ,  $R_1 = 200 \text{ k}\Omega$ ,  $R_2 = 500 \text{ k}\Omega$ ,  $R_3 = 1 \text{ M}\Omega$  in the above figure, what is the output voltage?

$$V_o = -R_f \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right) = -1\text{M} \left( \frac{-2}{200\text{k}} + \frac{3}{500\text{k}} + \frac{1}{1\text{M}} \right) = 3 \text{ V}$$



Output voltage:

$$V_o = -R_f \left( \frac{V_1}{R_1} + \dots + \frac{V_n}{R_n} \right)$$

# Non-Inverting Amplifier


Amp. não-inversor

- Assuming  $R_i = \infty$  and  $R_o = 0$ :

$$V_+ = V_1 \text{ and } V_- = \frac{R_1}{R_1 + R_f} V_o$$

$$V_o = A_v(V_+ - V_-) = A_v \left( V_1 - \frac{R_1}{R_1 + R_f} V_o \right) \rightarrow$$
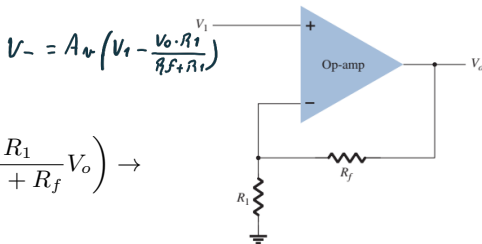
$$V_o = \frac{V_1}{1/A_v + R_1/(R_1 + R_f)}$$



- If  $A_v \gg 1$

$$V_o = \frac{R_1 + R_f}{R_1} V_1$$

- Output voltage:

$$V_o = \frac{R_1 + R_f}{R_1} V_1 = \left( 1 + \frac{R_f}{R_1} \right) V_1$$

- Example:** If  $R_1 = 100 \text{ k}\Omega$  and  $R_f = 500 \text{ k}\Omega$  in the above figure, what output voltage results for an input of  $V_1 = 2 \text{ V}$ ?

$$V_o = \left( 1 + \frac{R_f}{R_1} \right) V_1 = \left( 1 + \frac{500\text{k}}{100\text{k}} \right) \times 2 = 12 \text{ V}$$

# Unit Gain Follower and Unit Gain Inverter


↳ Amp. com ganho unitário

Por que isso esse se não invade  
nem amplifica (ganho unitário)?  
Porque eu posso querer  
isolar uma porção do circuito

## ► Unit Gain Follower

- Non-inverting amplifier with unit gain:


$$V_o = V_1$$

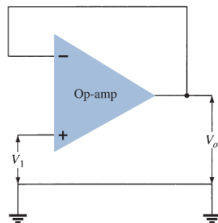

## ► Unit Gain Inverter

- Inverting amplifier with unit gain:

$$V_o = -V_1$$

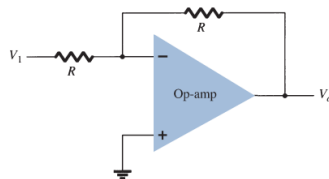


# Integrator → acumular um erro com o tempo

2º o que usa  
integral na  
fórmula

- Remembering that  $V_- = 0$ :

$$i = \frac{v_1}{R} = -C \frac{dv_o}{dt}$$
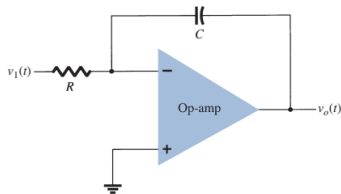
$$v_o(t) = -\frac{1}{RC} \int_0^t v_1(\tau) d\tau$$



- Note:** integration operation sums the area under a waveform over a period of time
- If a fixed voltage is applied as input, the output voltage grows linearly, producing a ramp voltage
- The output voltage ramp is opposite in polarity to the input voltage and is multiplied by  $1/RC$
- If  $v_1 = 1$  V,  $R = 1$  M $\Omega$  and  $C = 1$   $\mu$ F, the output ramp voltage grows  $-1$  V/s
- If  $v_1 = 1$  V,  $R = 100$  k $\Omega$  and  $C = 1$   $\mu$ F, the output ramp voltage grows  $-10$  V/s



# Differentiator

↳ controlar aceleração  
com o tempo


Diferenciador  
×  
Integrador } Depende de onde o  
capacitor e' posto.

- ▶ Remembering that  $V_- = 0$ :

$$i = C \frac{dv_1}{dt} = -\frac{v_o}{R}$$

$$v_o(t) = -RC \frac{dv_1}{dt}$$

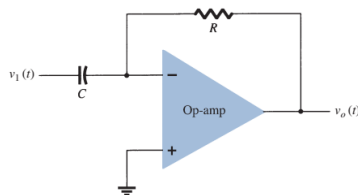- ▶ **Note:** differentiation operation gives the rate at which the input waveform changes with respect to time



# Specifications and Parameters

*Input offset voltage*

*Offset  $\rightarrow V_I$  necessária para que  $V_o = 0$*

- ▶ **Input Offset Voltage:** differential DC voltage required between the inputs to make the output zero
  - ▶ Ideally, the op-amp output should be 0 V when the input is 0 V; however there is some offset voltage at the output
  - ▶ Typical values range from mV down to  $\mu\text{V}$
- ▶ **Input Offset Current:** is equal to the difference between the input bias current at the non-inverting terminal minus the input bias current at the inverting
  - ▶ Ideally, input bias currents are zero and therefore the input offset current is also zero
  - ▶ Typical values range from nA (BJT Op-Amps) down to pA (MOSFET Op-Amps)
- ▶ **Open-Loop Gain:** gain obtained when no feedback is used in the circuit  
 *$\rightarrow$  Ganho de tensão em malha aberta*
- ▶ **Input Impedance:** given as common mode input impedance (static) and differential input impedance (dynamic with V and I)
- ▶ **Output Impedance:** decreases with feedback  
 *$\rightarrow$  Idealmente 0  $\Omega$ . Fornecida pelo fabricante*
- ▶ **Frequency Response:** given as *bandwidth* or *gain bandwidth product*
- ▶ **Slew-Rate:** maximum rate at which amplifier output can change in volts per microsecond  
 *$\rightarrow$  O tempo que leva para a tensão variar*

# Application Examples

## ► Constant-Gain Multiplier

### ► Inverting Circuit

► Voltage Gain:  $G = -\frac{R_f}{R_1}$


► Example:  $G = -\frac{200\text{k}}{2\text{k}} = -100$   
 $V_o = GV_i = -100 \times 2.5\text{m} = -250\text{ mV}$

$$G = -\frac{R_f}{R_1}$$

$$G = \frac{200\text{k}}{2\text{k}} = -100$$

$$V_o = G \cdot V_i = -100 \cdot 2.5\text{mV}$$

$$V_o = -250\text{mV}$$

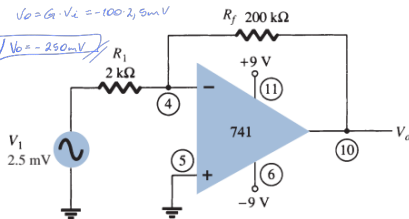


### ► Non-Inverting Circuit

► Voltage Gain:  $G = 1 + \frac{R_f}{R_1}$

► Example:  $G = 1 + \frac{240\text{k}}{2.4\text{k}} = 101$   
 $V_o = GV_i = 101 \times 120\mu = 12.1\text{ mV}$
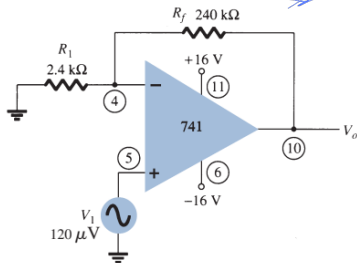
$$G = 1 + \frac{R_f}{R_1}$$
$$G = 1 + \frac{240\text{k}}{2.4\text{k}} = 1 + 100 = 101$$
$$V_o = G \cdot V_i = 101 \cdot 120\mu\text{V} = \frac{12120}{1000}\mu\text{V}$$
$$V_o = 12.12\text{mV}$$



# Application Examples

## ► Multiple-Stage Multiplier

► Voltage Gain:  $G = G_1 G_2 \dots G_n$


► Example:  $G = G_1 G_2 G_3 = \left(1 + \frac{470\text{k}}{4.3\text{k}}\right) \left(-\frac{470\text{k}}{33\text{k}}\right) \left(-\frac{470\text{k}}{33\text{k}}\right) = 22.4 \times 10^3$   
 $V_o = G V_i = 22.2 \times 10^3 \times 80\mu\text{V} = 1.79\text{ V}$

$$G = G_1 \cdot G_2 \cdot G_3 \quad \left(1 + \frac{470}{4.3}\right) \cdot \frac{470}{33} \cdot \frac{470}{33} = 22,4 \cdot 10^3$$

$$G = 1 + \frac{R_f}{R_i} = \frac{470\text{k}}{4.3\text{k}} + 1$$

$$G = -\frac{470\text{k}}{33\text{k}}$$

$$G = -\frac{470\text{k}}{33\text{k}}$$

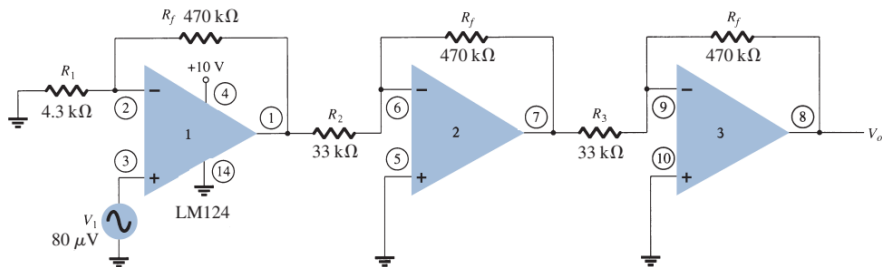

$$V_o = G \cdot V_i$$

$$V_o = 22,4 \cdot 10^3 \cdot 80\mu\text{V}$$

$$V_o = 1,79\text{ V}$$

# Application Examples


## ► Voltage Summing

### ► Output Voltage:

$$V_o = - \left( \frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \cdots + \frac{R_f}{R_n} V_n \right)$$
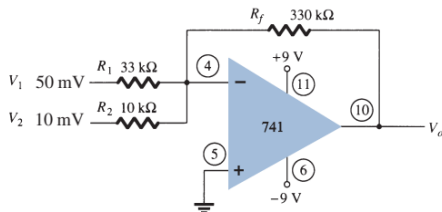
### ► Example:


$$V_o = - \left( \frac{330\text{k}}{33\text{k}} 50\text{m} + \frac{330\text{k}}{10\text{k}} 10\text{m} \right) = 830 \text{ mV}$$



## ► Voltage Buffer

### ► Output Voltage:

$$V_o = V_i$$


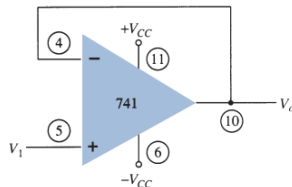


# Application Examples
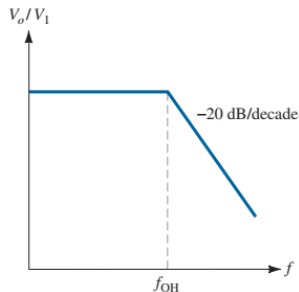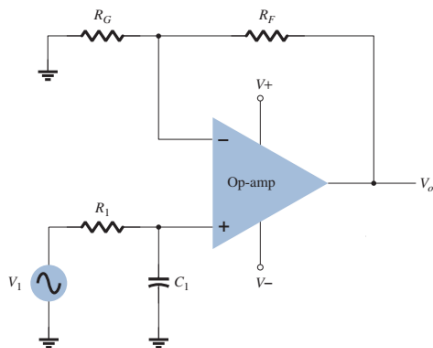
## ► Low-Pass Filter

► Voltage Gain:  $G = 1 + \frac{R_F}{R_G}$

► Cutoff Frequency:  $f_{OH} = \frac{1}{2\pi R_1 C_1}$





# Application Examples
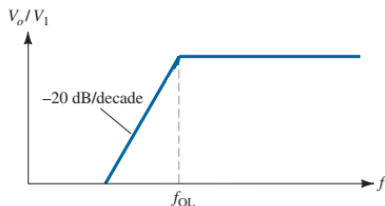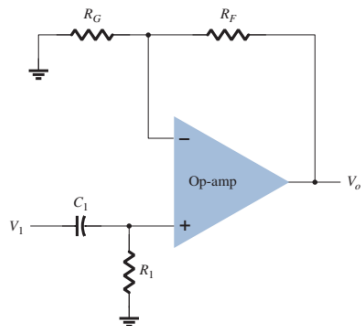
## ► High-Pass Filter

► Voltage Gain:  $G = 1 + \frac{R_F}{R_G}$

► Cutoff Frequency:  $f_{OL} = \frac{1}{2\pi R_1 C_1}$



# Application Examples

## ► Band-Pass Filter

