

# 6872 Foundations of Electronics

## Lecture 10: Power Amplifier

Elvio J. Leonardo

Bachelor Degree in Computer Science  
Department of Informatics  
State University of Maringá

v. 2020

# Abstract



- ▶ Power Amplifier Operation Classes
- ▶ Class A Operation
- ▶ Class B Operation

# Amplifiers


- ▶ Amplifier receives a signal from some input source and provides a larger version of the signal to some output device (or to another amplifier stage)
- ▶ Input signal is generally small (few microvolts (antenna) to few millivolts (audio transducer))
- ▶ **Small-signal amplifiers** (a.k.a. preamplifier or preamp) are usually concerned with amplification linearity and magnitude of gain
- ▶ Preamps are usually voltage amplifiers
- ▶ **Large-signal amplifiers** (a.k.a. power amplifiers) provide sufficient power to an output load (a speaker or other power device), typically from a few watts to tens of watts
- ▶ Power amplifier is generally the last stage of a multistage amplifier
- ▶ Power amplifiers are concerned power efficiency, distortion, maximum amount of power that the circuit is capable of handling, and impedance matching to the output device

Power efficiency:  $\eta = \frac{P_{out(ac)}}{P_{in(dc)}} \times 100\%$

# Load-Line and Q-Point



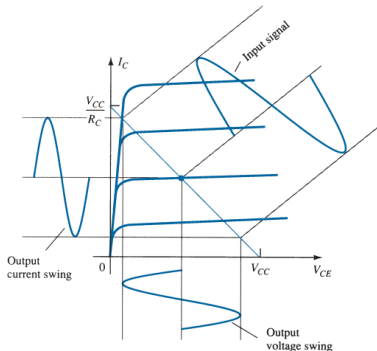
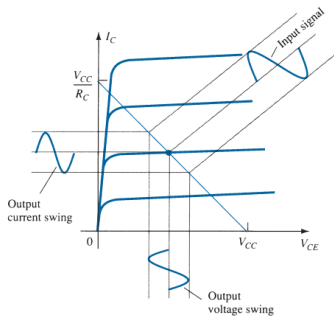


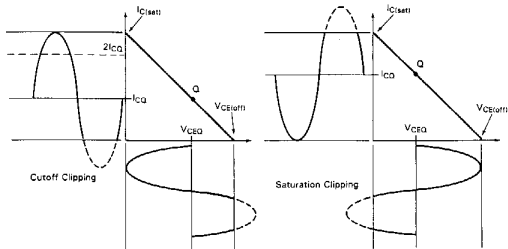- Load-line is limited by transistor saturation and cut-off
- The signal is clipped off if transistor saturates or cuts-off


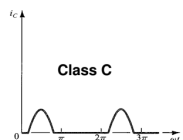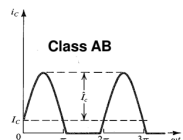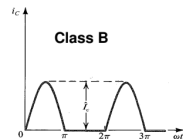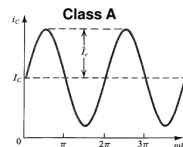
# Power Amplifiers Classes

- ▶ **Class A:** output signal varies for a full  $360^\circ$  of the input signal and the Q-point is around the middle of the active region
- ▶ **Class B:** output signal varies for one-half the input signal cycle, or for  $180^\circ$  of signal, and the Q-point is at 0 V
  - ▶ Two class B operations are required (one for the positive-output half-cycle and another for the negative-output half-cycle)
- ▶ **Class AB:** Q-point is above 0 V (class B) but below the middle of the active region (class A)
  - ▶ Also requires two operations (same as class B)
- ▶ **Class C:** output signal varies for less than  $180^\circ$  of signal
  - ▶ Used only in special areas, such as radio or communications
- ▶ **Class D:** operation using pulse (digital) signals, which are on for a short interval and off for a longer interval
  - ▶ Uses digital techniques to obtain a signal that varies over the full cycle




# Series-Fed Class A Amplifier Example

## ► Power considerations:

► Input DC Power:  $P_{in(DC)} = V_{CC} I_{C(Q)}$

► Output AC Max Power:  $P_{out(AC)} = \frac{V_{CE(pp)}}{2\sqrt{2}} \frac{I_{C(pp)}}{2\sqrt{2}} = \frac{V_{CC}}{2\sqrt{2}} \frac{2I_{C(Q)}}{2\sqrt{2}} = \frac{V_{CC} I_{C(Q)}}{4}$

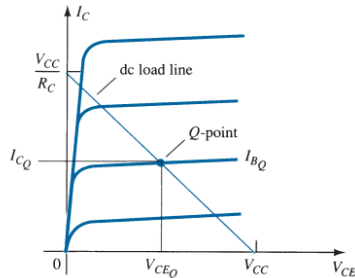► Max Efficiency:  $\eta = \frac{V_{CC} I_{C(Q)}/4}{V_{CC} I_{C(Q)}} = 25\%$



## ► Example


►  $I_{B(Q)} = \frac{V_{CC} - V_{BE}}{R_B} = \frac{20 - 0.7}{1k} = 19.3 \text{ mA}$

►  $I_{C(Q)} = \beta I_{B(Q)} = 25 \times 19.3m = 483 \text{ mA}$

►  $P_{in(DC)} = V_{CC} I_{C(Q)} = 20 \times 483m = 9.65 \text{ W}$



► Assuming  $\hat{I}_C = 250 \text{ mA}$ ,  $P_{out(AC)} = \left(\frac{\hat{I}_C}{\sqrt{2}}\right)^2 R_C = \left(\frac{250m}{\sqrt{2}}\right)^2 20 = 625 \text{ mW}$

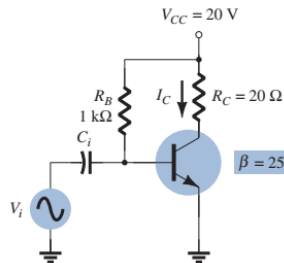►  $\eta = \frac{P_{out(AC)}}{P_{in(DC)}} = \frac{0.625}{9.65} = 6.5\%$



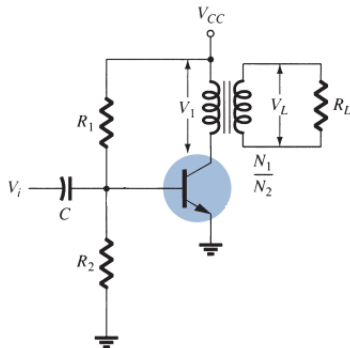
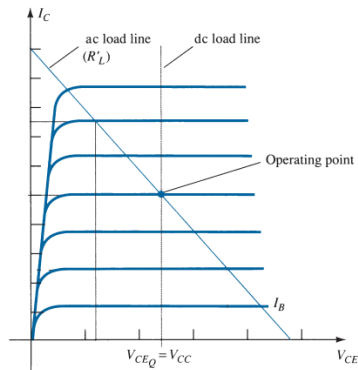
# Transformer-Coupled Class A Amplifier

- ▶ Lower DC power loss due to very small resistance of transformer primary coil
- ▶ Max Efficiency:  $\eta = 50\%$
- ▶ Reflected load resistance:  $R'_L = \left(\frac{N_1}{N_2}\right)^2 R_L$
- ▶ Note the difference between the DC and AC load-lines


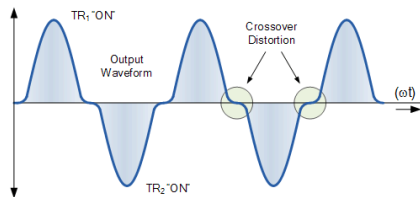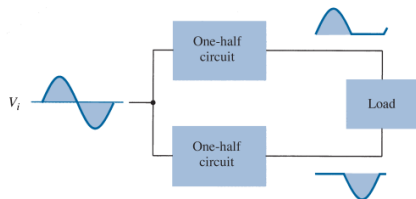
# Class B Amplifier


- ▶ DC bias leaves transistor on the edge of the active region
- ▶ Transistor turns on when the AC signal is applied
- ▶ Transistor conducts for only one-half of the signal cycle
- ▶ For the full cycle of signal, it is necessary to use two transistors, each conducting on opposite half-cycles
- ▶ This circuit is referred to as a **push-pull circuit**
- ▶ Max Efficiency:  $\eta = 78.5\%$
- ▶ **Crossover Distortion** caused by switching between transistors




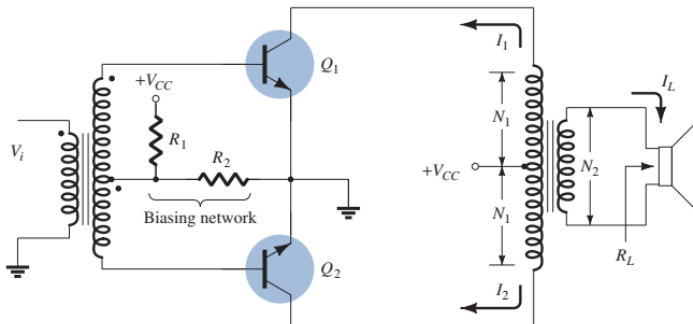
# Transformer Coupled Push-Pull Circuit

- ▶ First half-cycle of operation:
  - ▶ Transistor  $Q_1$  conducts, whereas transistor  $Q_2$  stays off
  - ▶ Current  $I_1$  through the transformer results in the first halfcycle of signal to the load
- ▶ Second half-cycle of operation:
  - ▶ Transistor  $Q_2$  conducts, whereas transistor  $Q_1$  stays off
  - ▶ Current  $I_2$  through the transformer results in the second halfcycle of signal to the load



# Complementary Push-Pull Circuit

- ▶ Uses complementary transistors (NPN and PNP types)
- ▶ The same signal is applied to the base of both transistors
- ▶ The transistors, being of opposite type, will conduct on opposite half-cycles of the input

